

Latches, Flip-Flops, and Registers

By Jake D. Karas

Lab 8 - Latches, Flip-Flops, and Registers

Jake D. Karas

U0000008780

11/28/2021

Objective:

The goal of this lab was to design three key components useful both in general and in the 4-bit CPU. The first of these, the D Latch, stores the previous output state of a section of a logic circuit, updating on a particular input level (0 or 1) of a clock input. A D Flip-Flop, however, functions similar to a D Latch, except for the fact that it only updates on a particular edge (a change in level) of said clock. The D Flip-Flop designed in this lab is negative-edge triggered, meaning that the output updates when the clock input changes from 1 to 0. Lastly, nine D-Flip-Flops were then connected to the same clock, but with separate D inputs and Q outputs. This formation serves as the instruction register for the 4-bit CPU.

Verilog Code:

D Latch:

```
1 module DLatch(D, En, Q);
2   input D, En;
3   output Q;
4   wire Dbar, T1, T2, Qbar;
5   not (Dbar, D);
6   nand (T1, D, En);
7   nand (T2, Dbar, En);
8   nand (Q, T1, Qbar);
9   nand (Qbar, T2, Q);
10  endmodule
```

D Flip-Flop:

```
1 module DFlipFlop(D, En, Q);
2   input D, En;
3   output Q;
4   wire EnBar, Y;
5   not (EnBar, En);
6   DLatch DL1 (D, En, Y);
7   DLatch DL2 (Y, EnBar, Q);
8   endmodule
```

D Flip-Flop Testbench:

```
1 module DFlipFlop_tb();
2   wire Q_out;
3   reg D_in, CLK;
4
5   DFlipFlop uut(.Q(Q_out), .D(D_in), .En(CLK));
6
7   initial
8   begin
9     D_in=1'b0;
10    CLK=1'b1;
11  end
12
13  always #50 CLK=~CLK;
14  always #85 D_in=~D_in;
15
16  endmodule
```

9-Bit Register:

Lab 8 - Latches, Flip-Flops, and Registers


Jake D. Karas

U0000008780

11/28/2021

```
1 module NineBitRegister (In, CLK, Out);
2   input[8:0] In;
3   input CLK;
4   output[8:0] Out;
5   DFlipFlop DFF0 (In[0], CLK, Out[0]);
6   DFlipFlop DFF1 (In[1], CLK, Out[1]);
7   DFlipFlop DFF2 (In[2], CLK, Out[2]);
8   DFlipFlop DFF3 (In[3], CLK, Out[3]);
9   DFlipFlop DFF4 (In[4], CLK, Out[4]);
10  DFlipFlop DFF5 (In[5], CLK, Out[5]);
11  DFlipFlop DFF6 (In[6], CLK, Out[6]);
12  DFlipFlop DFF7 (In[7], CLK, Out[7]);
13  DFlipFlop DFF8 (In[8], CLK, Out[8]);
14 endmodule
```

Simulation Waveform:

 

Discussion:

As demonstrated by the output waveform, the output of the D Flip-Flop designed in this lab is only updated at the negative edge of the clock. When it does update, the output is set to the same state as the D input. This allows logic circuit designers to store a particular signal state as well as delay the timing of when another circuit component receives a state change to synchronize input changes so that don't care states aren't achieved.