

Part 1:

MATLAB Program:

```
1- num=[1]; den=[0.01, 1];
2- X=tf(num,den);
3- step(X)
4- grid
5- title('System Response To Unit Step')
6- xlabel('t Sec')
7- ylabel('y(t) V')
```

$$1. \quad V_R + V_C = x(t) \quad Ri(t) + \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau = x(t) \quad Ri(t) + \frac{1}{CD} i(t) = x(t)$$

$$RDi(t) + \frac{i(t)}{C} = Dx(t) \quad \left(RD + \frac{1}{C}\right) i(t) = Dx(t) \quad i(t) = CDy(t)$$

$$\left(RD + \frac{1}{C}\right) (CDy(t)) = Dx(t) \quad (RCD^2 + D)y(t) = Dx(t) \quad (RCD + 1)y(t) = x(t)$$

$$2. \quad RC \frac{dy(t)}{dt} + y(t) = x(t) \quad RC(sY(s) - y(0)) + Y(s) = X(s) \quad \text{Let } y(0) \text{ be } 0.$$

$$RCsY(s) + Y(s) = X(s) \quad (RCs + 1)Y(s) = X(s) \quad H(s) = \frac{Y(s)}{X(s)} = \frac{1}{RCs + 1}$$


$$3. \quad ((10000)(1 * 10^{-6})s + 1)Y(s) = \frac{1}{s} \quad (0.01s + 1)Y(s) = \frac{1}{s}$$

$$Y(s) = \frac{1}{s(0.01s + 1)} = \frac{A}{s} + \frac{B}{0.01s + 1} \quad A = \frac{1}{s(0.01s + 1)} \Big|_{s=0} = \frac{1}{0+1} = 1$$


$$B = \frac{1}{s(0.01s + 1)} \Big|_{s=-100} = -\frac{1}{100} = -0.01$$

$$Y(s) = \frac{1}{s} - \frac{0.01}{0.01s + 1} = \frac{1}{s} - \frac{1}{s + 100}$$

$$y(t) = u(t) - e^{-100s}$$

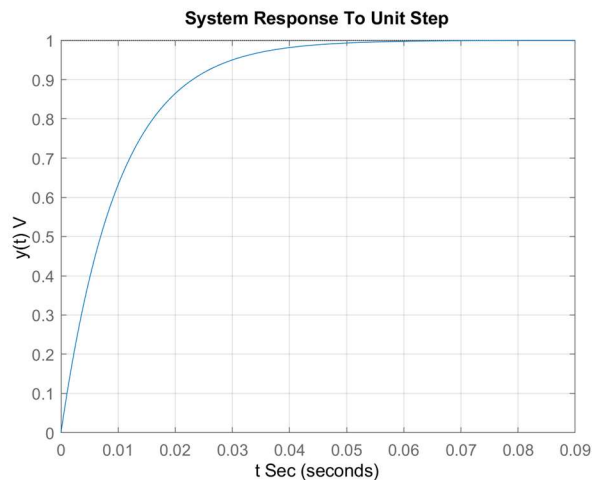

4.

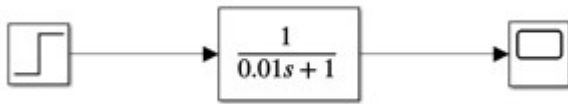

Part 2:

MATLAB Program:

```

1- L=10e-3; C=1e-6; R=[50 10 1 0.5 0];
2-
3- for i=1:5
4-     den=[L*C, R(i)*C, 1];
5-     roots(den)
6-     r=roots(den);
7-     figure(1)
8-     plot(r, 'o'); hold on;
9- end
10- xlim([-3000, 500])
11- ylim([-12000, 12000])
12- xlabel('Real')
13- ylabel('Imaginary')
14- grid
15-
16- figure(2)
17- R=50; %Toggle between all R values
18- num=[1]; den=[L*C R*C 1];
19-
20- G=tf(num,den);
21- step(G);
22- grid
  
```

$$1. \quad V_L + V_R + V_C = x(t) \quad L \frac{di(t)}{dt} + Ri(t) + \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau = x(t) \quad LDi(t) + Ri(t) + \frac{1}{CD} i(t) = x(t)$$

$$LD^2 i(t) + RDi(t) + \frac{i(t)}{C} = Dx(t) \quad \left(LD^2 + RD + \frac{1}{C} \right) i(t) = Dx(t) \quad i(t) = CDy(t)$$

$$\left(LD^2 + RD + \frac{1}{C} \right) (CDy(t)) = Dx(t) \quad (LCD^3 + RCD^2 + D)y(t) = Dx(t)$$

$$(LCD^2 + RCD + 1)y(t) = x(t) \quad LC \frac{d^2 y(t)}{dt^2} + RC \frac{dy(t)}{dt} + y(t) = x(t)$$


$$LC(s^2 Y(s) - sy(0) - y'(0)) + RC(sY(s) - y(0)) + Y(s) = X(s) \quad \text{Let } y(0) \text{ and } y'(0) \text{ be } 0.$$

$$LCs^2 Y(s) + RCsY(s) + Y(s) = X(s) \quad (LCs^2 + RCs + 1)Y(s) = X(s)$$

$$H(s) = \frac{Y(s)}{X(s)} = \frac{1}{LC^2 + RCs + 1} = \frac{1}{((10 \times 10^{-3})(10^{-6})) + (10^{-6})Rs + 1} = \frac{1}{10^{-8}s^2 + R \times 10^{-6}s + 1}$$

2.


| R Value (Ω) | Roots |
|----------------------|-----------------------------|
| 50 | $1000(-2.5 \pm j9.6825)$ |
| 10 | $1000(-0.5 \pm j9.9875)$ |
| 1 | $1000(-0.05 \pm j9.9991)$ |
| 0.5 | $1000(-0.025 \pm j10.0000)$ |
| 0 | $\pm j10000$ |

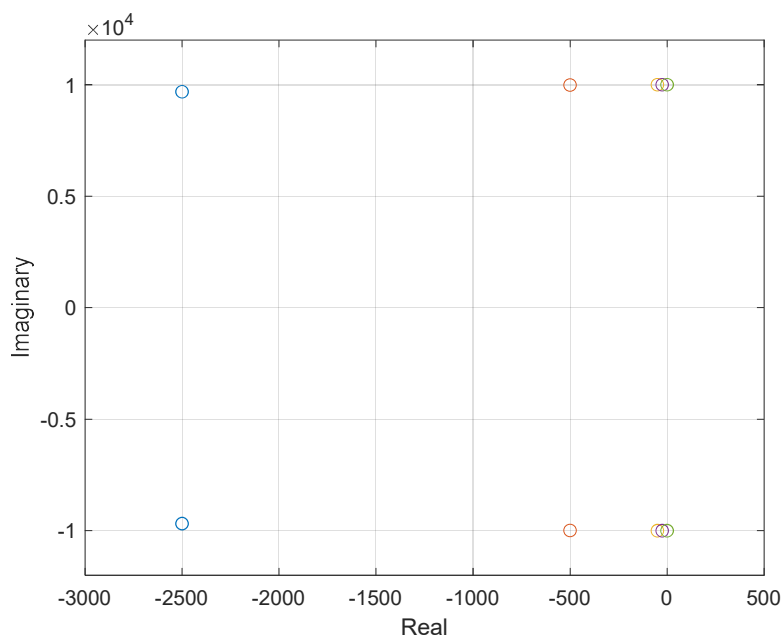


Decreasing the resistance decreases system stability.

3.


$R = 50 \, \Omega$:

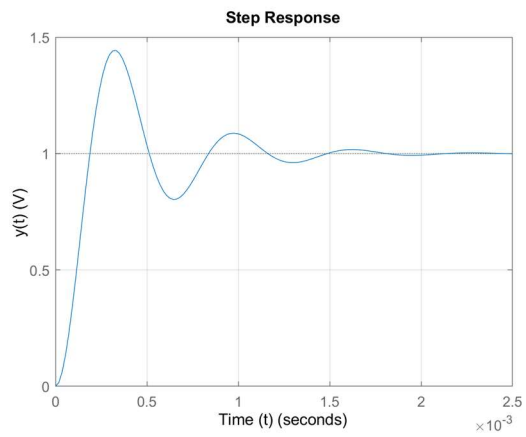


$R = 10 \, \Omega$:

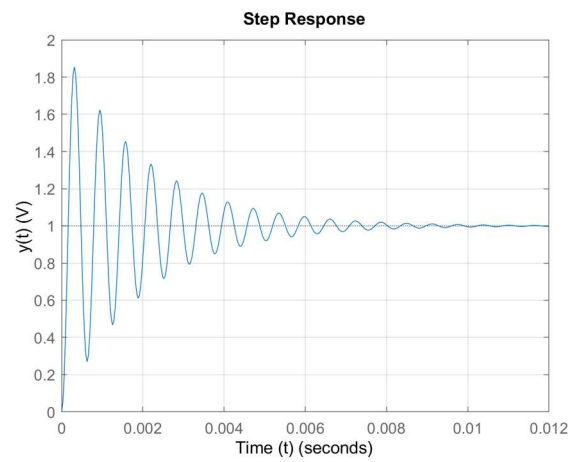


$R = 1 \, \Omega$:

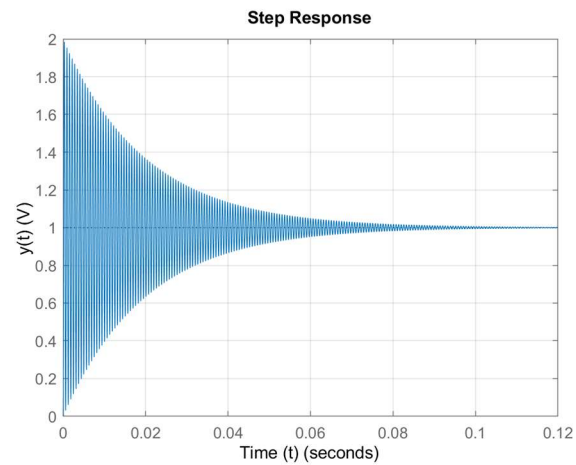

$R = 0.5 \Omega$:

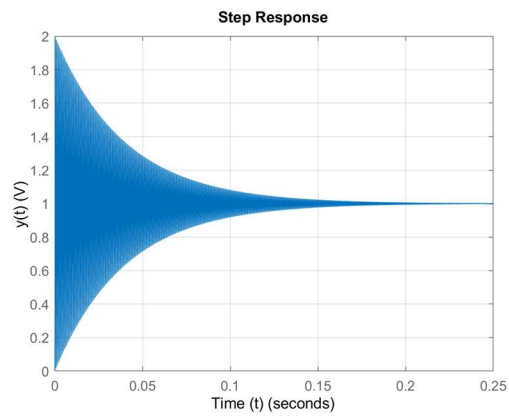


$R = 0 \Omega$:

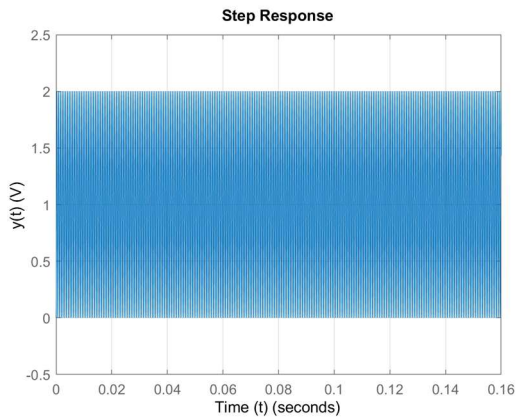

4. The further away from the complex axis (imaginary part = 0), the faster the signal dampens. When the poles are on the complex axis, the output oscillates permanently.

5.

Poles: $1000(0.05 \pm 9.9999i)$

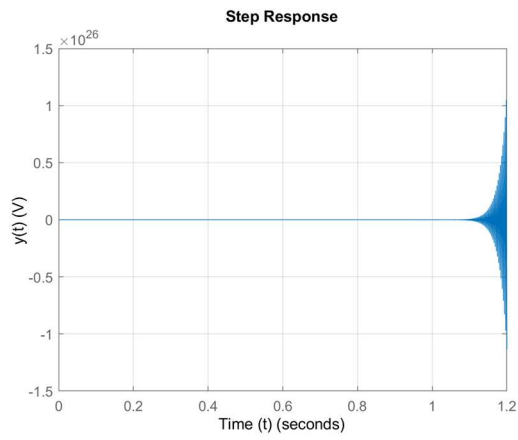

The system becomes unstable with negative resistance, with the magnitude of oscillation increasing infinitely.